



BASİT ELEKTRİK DEVRELERİ

⚙️ Aşağıda verilen devre elemanlarının adlarını yazınız.



.....



.....



.....



.....



.....



.....

⚙️ Aşağıda verilen devre elemanlarının görevlerini yazınız.



.....

.....

.....

.....

.....



.....

.....

.....

.....

.....



.....

.....

.....

.....

.....



.....

.....

.....

.....

.....



.....

.....

.....

.....

.....



.....

.....

.....

.....

.....